

# Lecture 10

---

Avi Herman

10/10/2024

## Table of Contents

---

- [Capacitors and Conductors](#)
  - [Capacitors](#)
  - [Conductors](#)
- [Batteries](#)
- [Current](#)
  - [Ohm's Law](#)
- [Resistance](#)
- [Electric Power](#)
- [Electric Circuits](#)
  - [Schematic Symbols](#)
  - [Types of Electric Circuits](#)
  - [Series and Parallel Circuit Diagrams](#)

## Capacitors and Conductors

---

### Capacitors

- **Capacitors** are devices that store energy in the form of an electric field.
  - At equilibrium, the electric field is zero and voltage and constant
  - Capacitance is the ability of a system to store charge.
- The capacitance of a capacitor is given by the formula:

$$C = \frac{Q}{V}$$

- Where
  - $C$  is the capacitance in farads (F),
  - $Q$  is the charge
  - $V$  is the voltage.
- The energy stored in a capacitor is given by the formula:

$$U = \frac{1}{2}CV^2$$

- Where
  - $U$  is the energy stored in the capacitor.

- See section [Schematic Symbols](#) for common capacitor symbols.

## Conductors

- **Conductors** are materials that allow the flow of electric current.
  - Conductors have a low resistance to the flow of electric current.

## Batteries

---

- **Batteries** are devices that store energy in the form of chemical energy.
  - They are used as a voltage source in electric circuits.
  - Most batteries are lithium-ion batteries.
    - They have LiCoO<sub>2</sub> cathodes (+) and graphite anodes (-).
    - They have an electrolyte that allows the flow of ions.
  - The voltage of a battery is the potential difference between the positive and negative terminals of the battery.
    - Thus measuring the voltage across terminals and then switching the terminals will give the negative of the original voltage.
- The energy stored in a battery is given by the formula:

$$E = VQ$$

- Where
  - $E$  is the energy stored in the battery.
  - $V$  is the voltage of the battery.
  - $Q$  is the charge.

## Current

---

- **Current** is the flow of electric charge.
  - The SI unit of current is the ampere  $A$  where  $A = \frac{C}{s}$ .

## Ohm's Law

- **Ohm's Law** states that the current flowing through a conductor is directly proportional to the voltage across the conductor and inversely proportional to the resistance of the conductor.
  - The formula for Ohm's Law is:

$$I = \frac{V}{R}$$

- Where
  - $I$  is the current in amperes (A).
  - $V$  is the voltage in volts (V).
  - $R$  is the resistance in ohms ( $\Omega$ ).

## Resistance

---

- **Resistance** is the opposition to the flow of electric current.
  - The SI unit of resistance is the ohm ( $\Omega$ ).
- The resistance of a conductor is given by the formula:

$$R = \frac{V}{I}$$

- Where
  - $R$  is the resistance in ohms ( $\Omega$ ).
  - $V$  is the voltage in volts (V).
  - $I$  is the current in amperes (A).
- *Resistors* are devices that are used to control the flow of electric current in a circuit.
  - See section [Schematic Symbols](#) for common resistor symbols.

## Electric Power

---

- **Electric Power** is the rate at which electric energy is transferred by an electric circuit.
  - The formula for electric power is:

$$P = IV$$

- Where
  - $P$  is the power in watts (W).
  - $I$  is the current in amperes (A).
  - $V$  is the voltage in volts (V).
- The energy consumed by an electric circuit is given by the formula:

$$E = Pt$$

- Where
  - $E$  is the energy consumed in joules (J).
  - $P$  is the power in watts (W).
  - $t$  is the time in seconds (s).


## Electric Circuits

---

- **Electric Circuits** are systems that allow the flow of electric current.
  - Electric circuits are made up of components such as resistors, capacitors, and batteries.

## Schematic Symbols

## Circuit Symbols

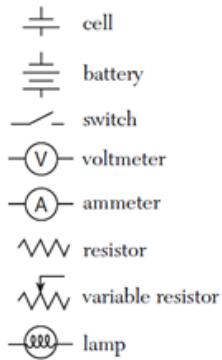

## Types of Electric Circuits

- There are two types of electric circuits:
  - **Series Circuits:** Components are connected in a single path.
    - Resistors in series add up to the total resistance.
    - $R_{\text{total}} = R_1 + R_2 + \dots + R_n$
  - **Parallel Circuits:** Components are connected in multiple paths.
    - Resistors in parallel add up to the reciprocal of the total resistance.
    - $\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$
- Larger circuits can be made up of series and parallel circuits.

## Series and Parallel Circuit Diagrams

